

Name.....

Roll No.....

DEPARTMENT OF ELECTRICAL ENGINEERING  
National Institute of Technology Calicut  
END SEMESTER EXAMINATION-DECEMBER 2013

ZZ 1003: Basic Electrical Sciences (Electrical)

Total Time for Electrical and Electronics: 3 hours.

Maximum: 25 Marks

Answer all questions

1. Using mesh analysis, find the current  $i_x$  in the circuit shown in Fig. 1. (2.5 marks)

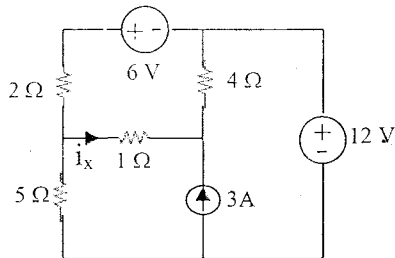


Fig.1

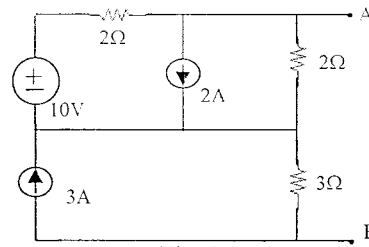


Fig. 2

2. Using superposition theorem, find the voltage across A and B. for the circuit shown in Fig.2. (2 marks)
3. In the circuit shown in fig.3 what value of  $R_L$  will absorb maximum power? Also find the maximum power absorbed by  $R_L$ . (3 marks)

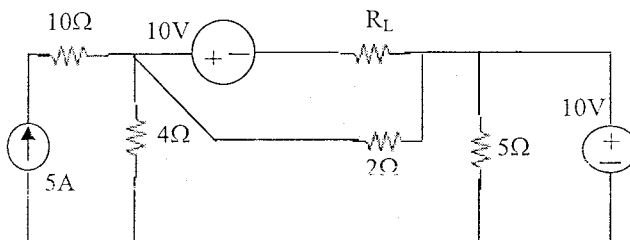


Fig. 3

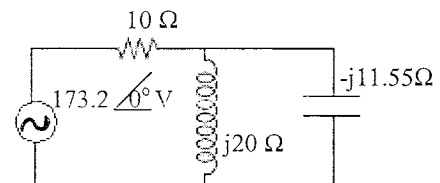


Fig. 4

4. Two coils A and B of 600 and 100 turns respectively are wound uniformly around a wooden ring of mean circumference 80 cm. The cross sectional area of the ring is 4 cm<sup>2</sup>. Calculate (a) self inductance of each coil (b) mutual inductance between the coils (c) emf induced in coil B when a current of 2 A in coil A is reversed in 0.01 second. (3 marks)
5. A parallel plate capacitor has its plates separated with a slab of 4 mm thickness having relative permittivity 3. If the capacitance is observed to be one third of the original value, when a second slab of 6 mm thickness is inserted in series with the first slab, what should be the relative permittivity of the second slab. (2 marks)
6. Calculate the rms value and the form factor of a symmetric alternating voltage signal  $v(t)$  which increases linearly from 0 to 200 V in the first millisecond, holds at 200 V for the next 2 milliseconds and then decreases linearly to 0 V in the fourth millisecond of its +ve half cycle. (2 marks)
7. For the circuit shown in Fig.4, evaluate the current through and voltage across each element. Draw the phasor diagram. (3 marks)
8. The potential difference measured across a coil is 20 V with a direct current of 2A and it is 140 V with an alternating current of 2A at 40 Hz. If the coil is connected to a 230 V 50 Hz supply, calculate (a) the current (b) the active power (c) the reactive power and (d) the power factor. (3 marks)
9. The sinusoidal current through a circuit with a supply voltage of 100  $\angle 0^\circ$  V at 50 Hz is given by  $(3+j4)A$ . If the circuit comprises of two elements, identify the elements and their values. (2 marks)
10. Three alternating quantities are given as  $A = 40 \sin(\omega t)$ ,  $B = 60 \sin(\omega t - \pi/2)$  and  $C = (10 \sin \omega t - 17.3 \cos \omega t)$ . Draw a phasor diagram showing the above three quantities taking  $\sin(\omega t - \pi/6)$  as the reference. Find the resultant and express the resultant in exponential form. (2 marks)
11. An alternating current is represented by  $i = 12 + 100 \sin(628t + 30^\circ)A$ . Find the time taken for the current to reach a value of 80 A for the first time. (0.5 mark)


National Institute of Technology Calicut  
Department of Electronics and Communications Engineering  
End Semester Examination (Monsoon 2013)  
ZZ1003- Basic Electrical Sciences (Electronics Part)

Time: 1.5 hours


Answer All Questions

Max. Marks: 25

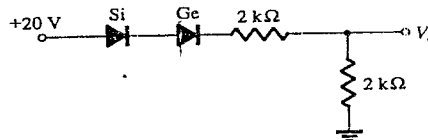1. Determine the level of  $V_o$  for the network (consider diode drops) [2 Marks]




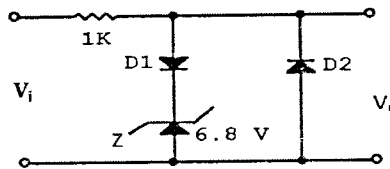2. In the following circuit, an input voltage  $V_i = 10\sin(100\pi t)$  is applied. Assume that the diode drop is 0.7 V when it is forward biased. The Zener breakdown voltage is 6.8V. Find the maximum and minimum values of output voltage. [2 Marks]




3. Determine the given parameters for the circuit shown in figure below [3 Marks]

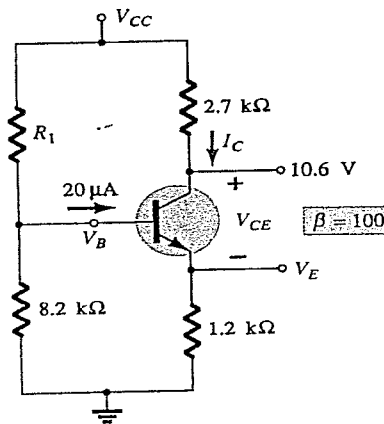- (a)  $I_C$   
(b)  $V_E$   
(c)  $V_{CC}$   
(d)  $V_{CE}$   
(e)  $V_B$   
(f)  $R_1$



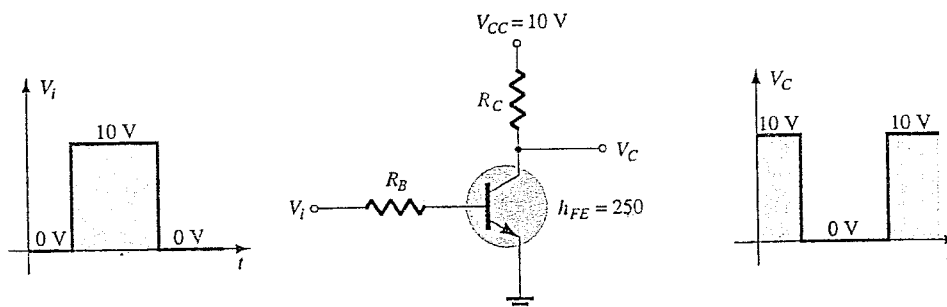4. Determine  $R_B$  and  $R_C$  for the circuit shown in figure, If  $I_{Csat} = 10$  mA. [2 Marks]



5. In each case of the following operations determine the base of the numbers so that the given expressions are true [2 Marks]
- (a)  $14/2 = 5$  (b)  $24 + 17 = 40$ .
6. Perform subtraction on the given binary numbers using the 2's complement [2 Marks]
- (a)  $10011-10010$  (b)  $100010-100110$
7. Simplify the following expressions using K-map [3 Marks]
- (a)  $\sum (9, 10, 12) \text{ \& } d(3, 5, 6, 7, 11, 13, 14, 15)$   
 (b)  $\prod (1, 4, 5, 11, 12, 14) \text{ \& } d(6, 7, 15)$
8. Implement the following four Boolean expressions with three half adders: [2 Marks]
- $$D = A \oplus B \oplus C$$
- $$E = A'BC + AB'C$$
- $$F = ABC' + (A' + B')C$$
- $$G = ABC$$
9. Implement the Boolean function [2 Marks]
- $$F = xy + x'y' + y'z$$
- (a) With NAND and inverter gates  
 (b) With NOR and inverter gates
10. Design a combinational circuit that takes 2-bit number  $X=X_1X_0$ , and computes the square of that number  $Y=X^2$  (Eg: if  $X = 10$  then  $Y = 0100$ ). [3 Marks]
11. Explain the function of horizontal and vertical deflection plates in Cathode Ray Oscilloscope [2 Marks]